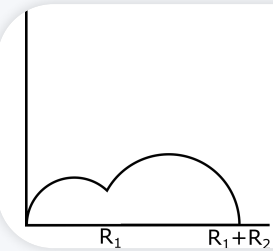


What impedance response might you expect from the equivalent circuit shown?



1




70%

35




2

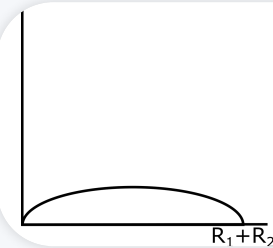

22%

11


3

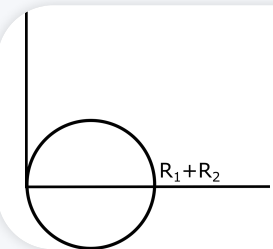

4%

2

4

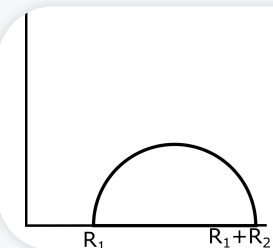

4%

2